
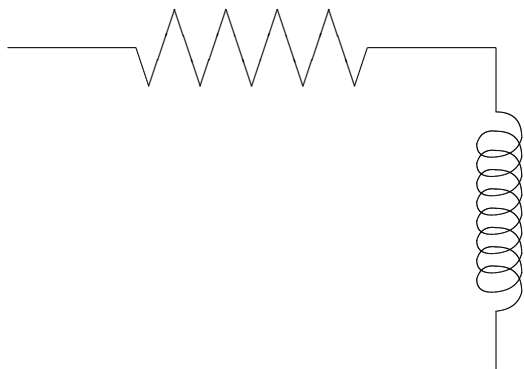



# The Governing Equation of an LRC Series Circuit


Bernd Schröder

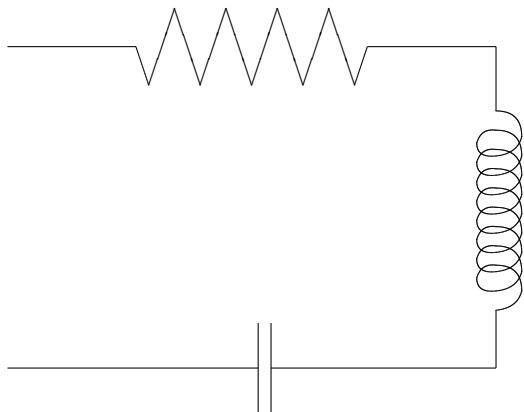






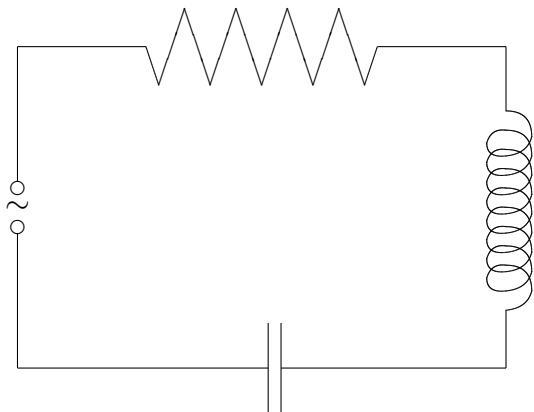


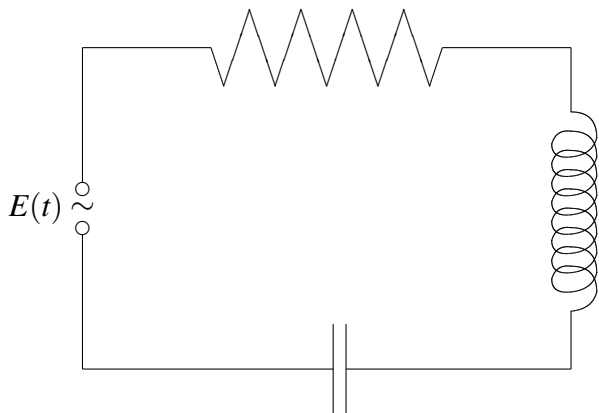

$$E(t) =$$

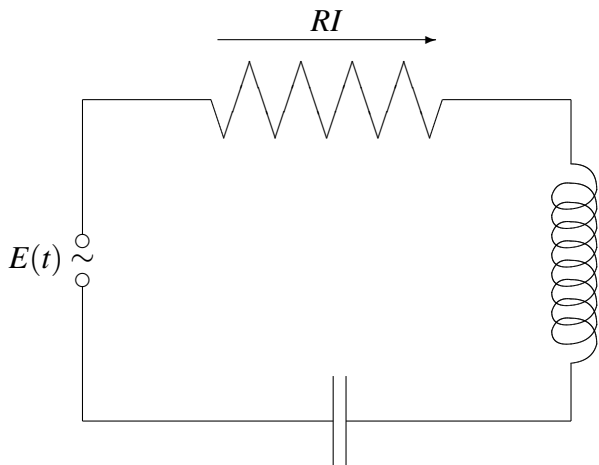


$$E(t) = RI$$

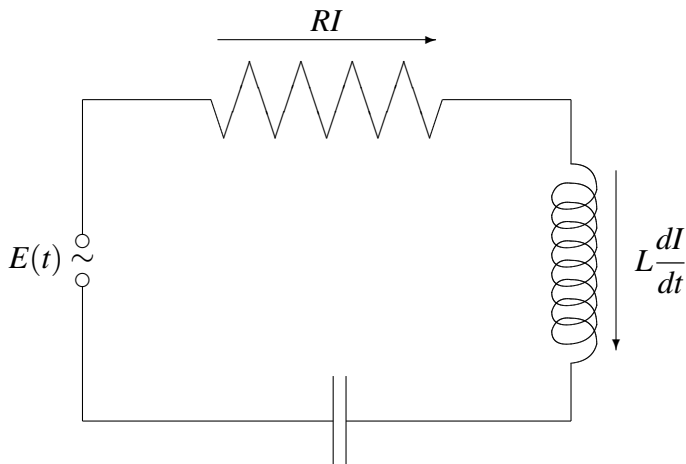


$$E(t) = L \frac{dI}{dt} + RI$$




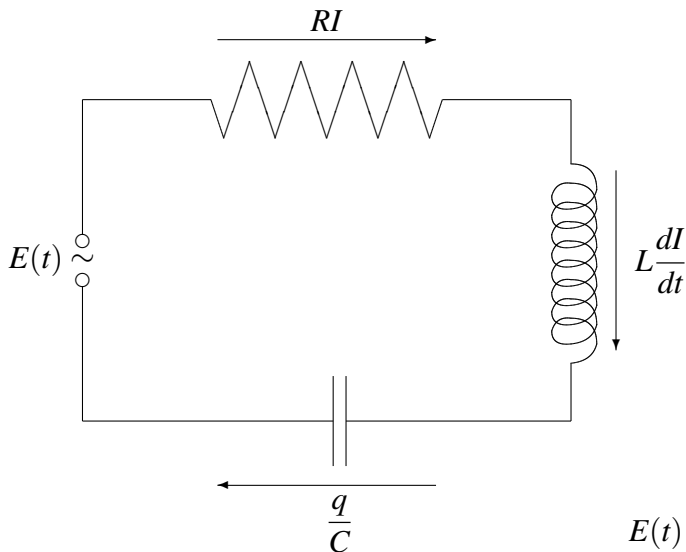

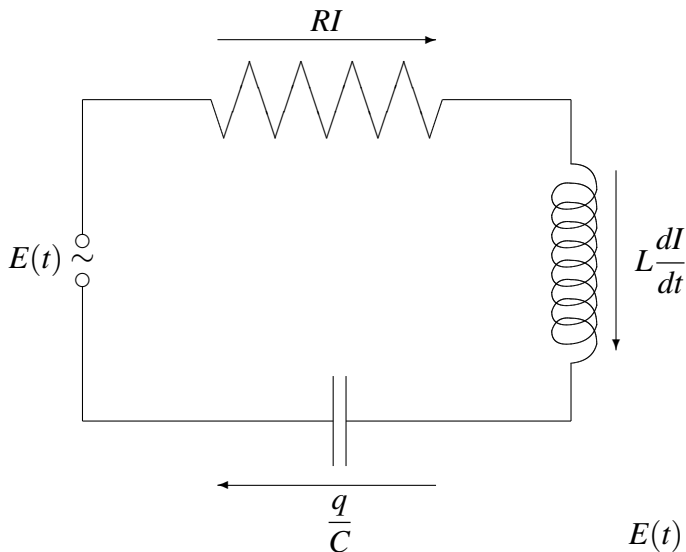
$$E(t) = L \frac{dI}{dt} + RI + \frac{q}{C}$$


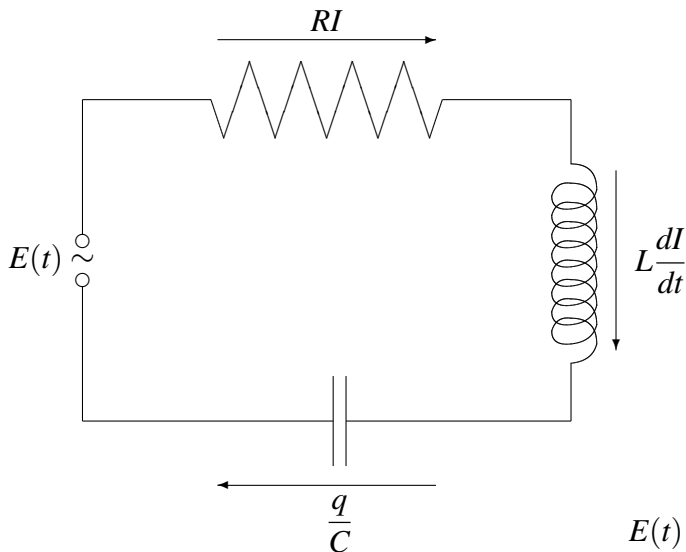
$$E(t) = L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q$$


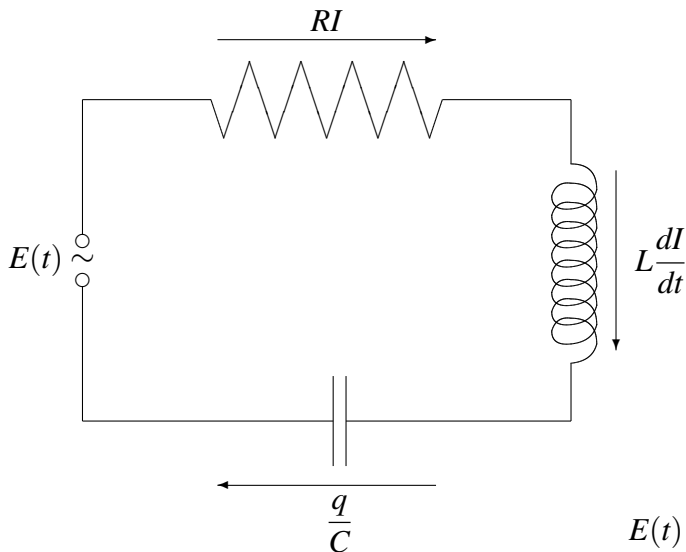
$$E(t) = L \frac{dI}{dt} + RI + \frac{q}{C}$$



$$E(t) = L \frac{dI}{dt} + RI + \frac{1}{C} \int I dt$$